



---

---

# Single Cycle Processor

---

## Chapter 4

---

---



# Single Cycle Processor

- ★ Design Concept
- ★ Design Steps
- ★ Instruction Set Architecture (nanoLADA)
- ★ Components
  - Register Files
  - Extender
  - Memory
- ★ Data Path
- ★ Control Signal
- ★ Critical Path



# Design Concept

★ Performance (CPU Time)  
is a function of

- Instruction Count
- Cycle per Instruction
- Clock Cycle Time

Depends on:  
Programs  
ISA  
Compiler

Instruction Count

Depends on:  
Programs  
ISA  
Compiler?  
**CPU Organization**

Cycle Per  
Instruction

Depends on:  
**CPU Organization**  
VLSI Technology

Clock Cycle  
Time



## Design Concept (ctd.)


- ★ Processor Design (DataPath and Control) will determine:
  - Cycle Per Instruction
  - Clock Cycle Time
- ★ We will (try to) design a single-cycle processor
  - 1 cycle per instruction (simple)
  - Very long cycle time (slow)
- ★ In hope that you will understand the internal organization of the processor



## Design Concept (ctd.)
 
### ★ Single-Cycle Processor (CPU = 1)

- Start an instruction every cycle.
- Related operation for an instruction is a combinational logic.





# Design Steps


1. Analyze the ISA to determine datapath requirements
  - a. Definition of each instruction on Register Transfer Language (RTL)
  - b. Storage Elements (registers, and more)
2. Select set of datapath components and establish clocking methodology
3. Assemble datapath meeting the requirements
4. Analyze implementation of each instruction to determine setting of control points that effects the register transfer.
5. Assemble the control logic

Compare to to software design?


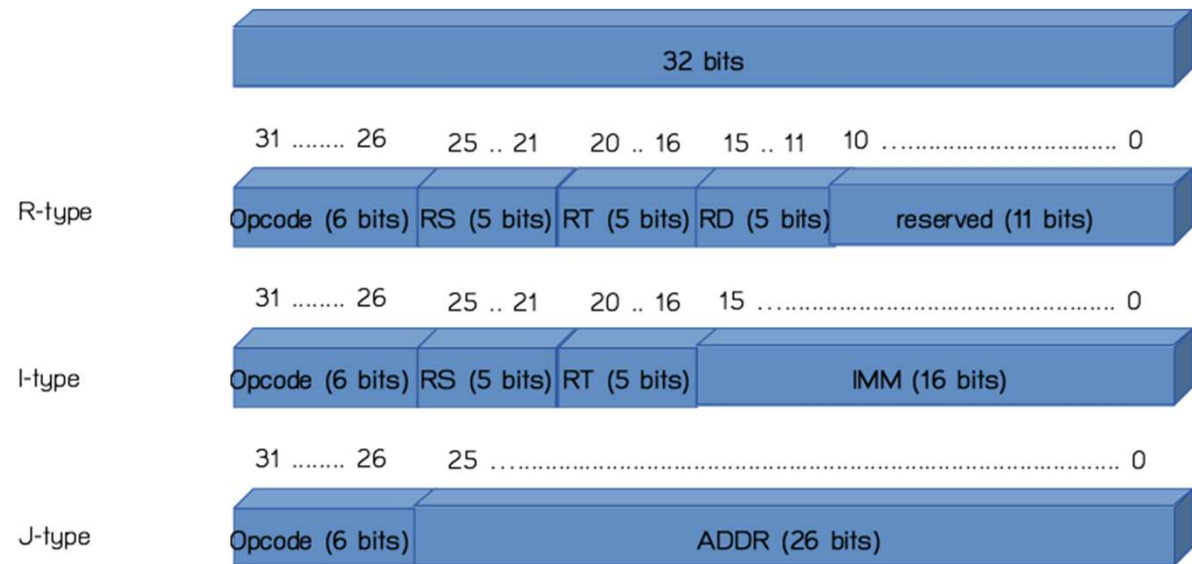
# Instruction Format (nanoLADA)

- ★ Fixed-Length
- ★ 3 formats
- ★ R-Type
  - 6-bit opcode
  - 5-bit RS, 5-bit RT, 5-bit RD
  - 11-bit reserve
- ★ I-Type
  - 6-bit opcode
  - 5-bit RS, 5-bit RT
  - 16-bit immediate
- ★ J-Type
  - 6-bit opcode
  - 26-bit address/displacement





# Step 1: Requirements (nanoLADA)

- ★ Instructions are explained with RTL.
- ★ ORI rt, rs, imm ; (I-type) ; Opcode 010000
  - $R[rt] \leftarrow R[rs] \mid \text{zero\_ext}(\text{imm});$
  - $PC \leftarrow PC + 4$
- ★ ORUI rt, rs, imm ; (I-type) ; Opcode 010001
  - $R[rt] \leftarrow R[rs] \mid \text{zero\_pad}(\text{imm});$
  - $PC \leftarrow PC + 4$
- ★ ADD rd, rs, rt ; (R-type) ; Opcode 000001
  - $R[rd] \leftarrow R[rs] + R[rt];$
  - $PC \leftarrow PC + 4$





## Step 1: Requirements (nanoLADA) (ctd.)

- ★ LW  $rt, imm(rs)$  ; (I-type) ; Opcode 011000
  - $R[rt] \leftarrow MEM[R[rs] + sign\_ext(imm)]$ ;
  - $PC \leftarrow PC + 4$
- ★ SW  $rt, imm(rs)$  ; (I-type) ; Opcode 011100
  - $MEM[R[rs] + sign\_ext(imm)] \leftarrow R[rt]$ ;
  - $PC \leftarrow PC + 4$



## Step 1: Requirements (nanoLADA) (ctd.)

- ★ BEQrs, rt, imm\*4 ; (I-type) ; Opcode 100100
  - If ( $R[rs] == R[rt]$ ) then
  - $PC \leftarrow PC + 4 + (\text{sign\_ext}(\text{imm}) * 4)$
  - else
  - $PC \leftarrow PC + 4$
- ★ JMP addr\*4 ; (J-type) ; Opcode 110000
  - $PC \leftarrow (\text{addr} * 4)$




## Step 2: Components for Datapath

- ★ Register file (bits? size?)
  - Indexed by RS, RT, RD
- ★ Special register
  - PC
- ★ ALU
  - Supports for ADD, OR
- ★ ADDER (for PC)
- ★ EXTENDER
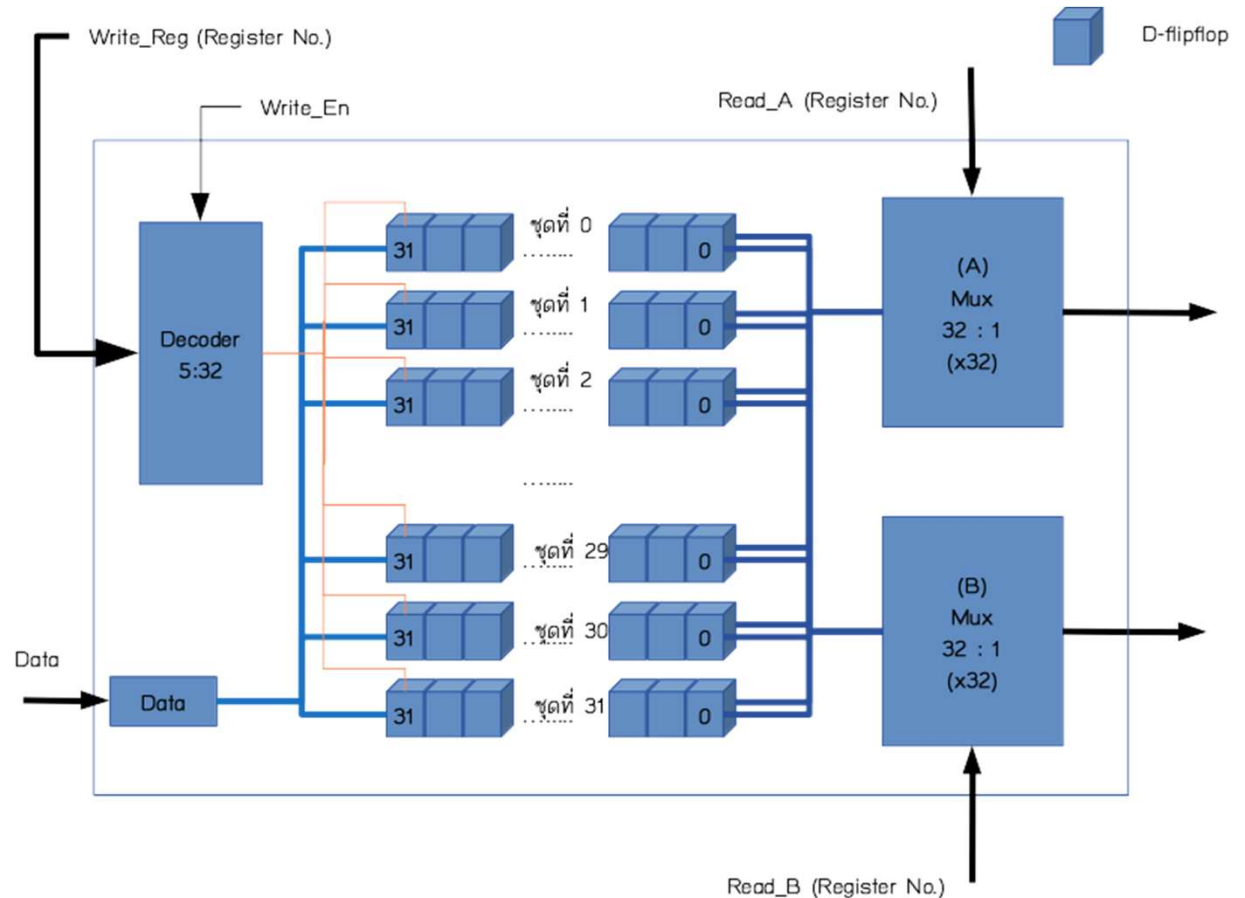
# Register File


- ★ 32 (5-bit address) registers
  - Each with 32 bit
- ★ Reading from 2 ports (Read\_A, Read\_B)
- ★ Writing to one port at Write\_Reg
- ★ Can be implemented with 32x32 D-flipflop, 2x multiplexors, and decoder




 
# Extender


- ★ Extend 16-bit immediate to 32-bit data
- ★ 3 modes
- ★ Sign Extender (b)
  - Extended with sign bit
- ★ Zero Padding (c)
  - Padded with 16'b0
- ★ Zero Extender (a)
  - Extended with 16'b0




 
# Memory

- ★ A memory
- ★ 32-bit in, out
- ★ 32-bit address
- ★ One port for read
- ★ One port for write





# ALU

- ★ Let's make an ALU that can
  - Add, Or, Sub

alu\_ops operations

00                       $S \leftarrow A + B$

01                       $S \leftarrow A | B$

10                       $S \leftarrow A - B$




## Step 3: Assembly Data Path

- ★ To assembly data path, simple add one instruction at a time
- ★ For each instruction added, modify the data path to support the RTL of the instruction.



# Complete Data Path

 



# Fetch and PC

- ★ Fetch is usually ignored by RTL.

- $\text{Instruction} \leftarrow \text{MEM}[\text{PC}]$
- $\text{PC} \leftarrow \text{PC} + 4$


- ★ Note.

$\text{PC} \leftarrow \text{PC} + 4$

also means

$\text{PC} \leftarrow \{\text{PC}[31:2] + 1, 2'b00\}$


We can use 30-bit adder for it.

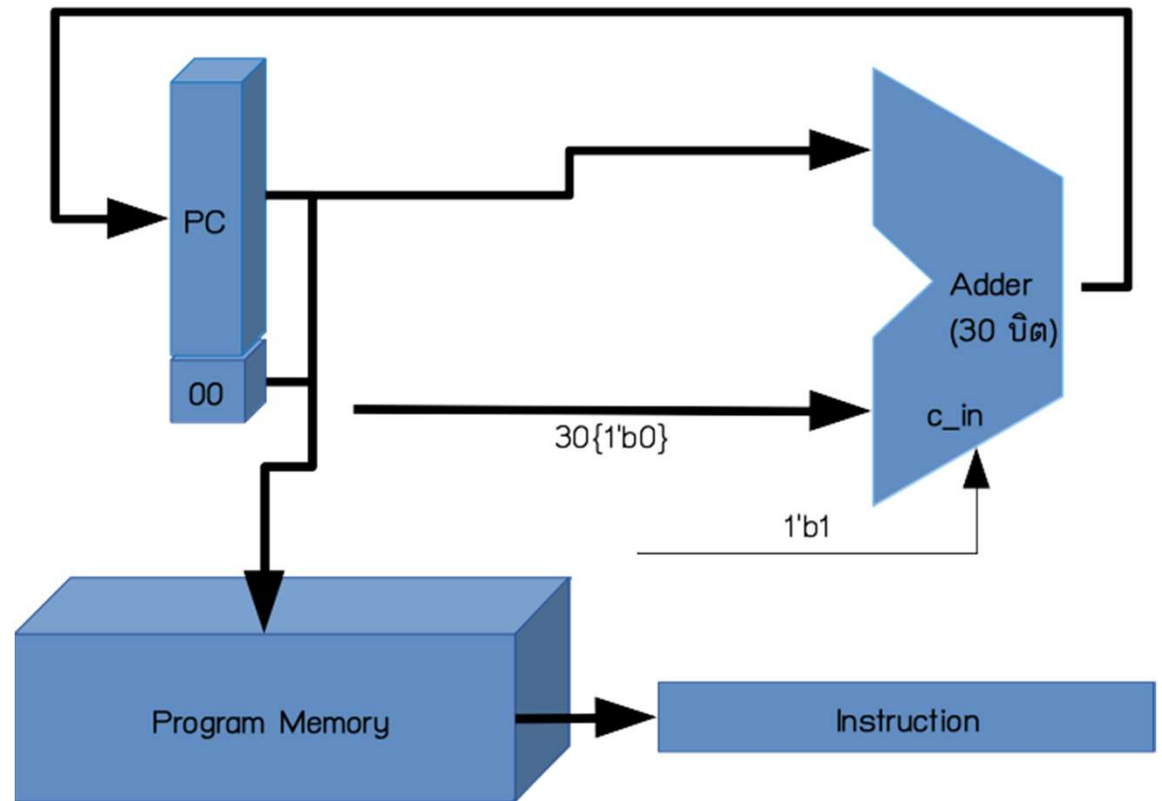


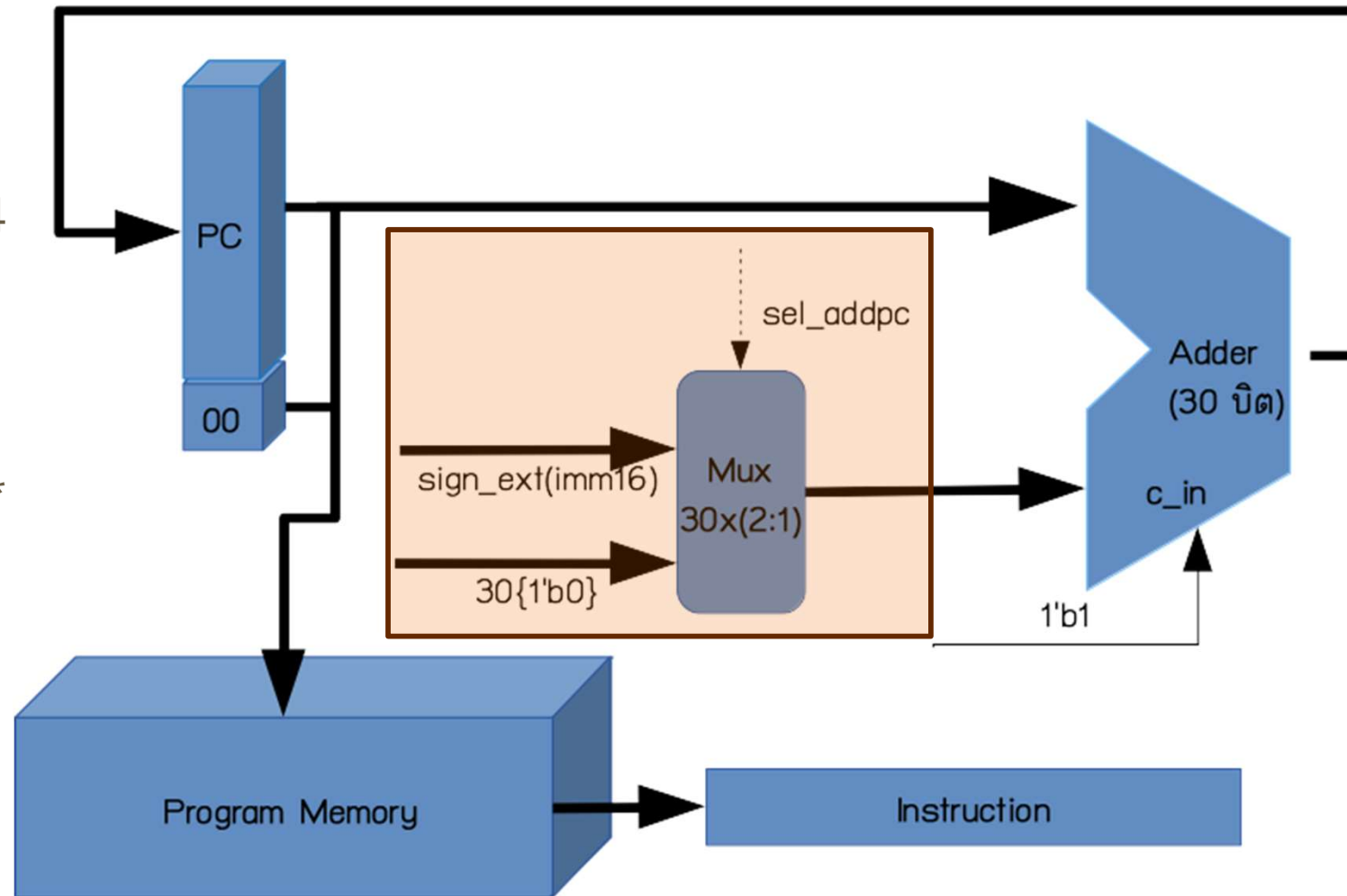
# BEQ


- ★ BEQrs, rt, imm\*4  
; (I-type)
  - If ( $R[rs] == R[rt]$ ) then
  - $PC \leftarrow PC + 4 + (\text{sign\_ext}(\text{imm}) * 4)$
  - else
  - $PC \leftarrow PC + 4$


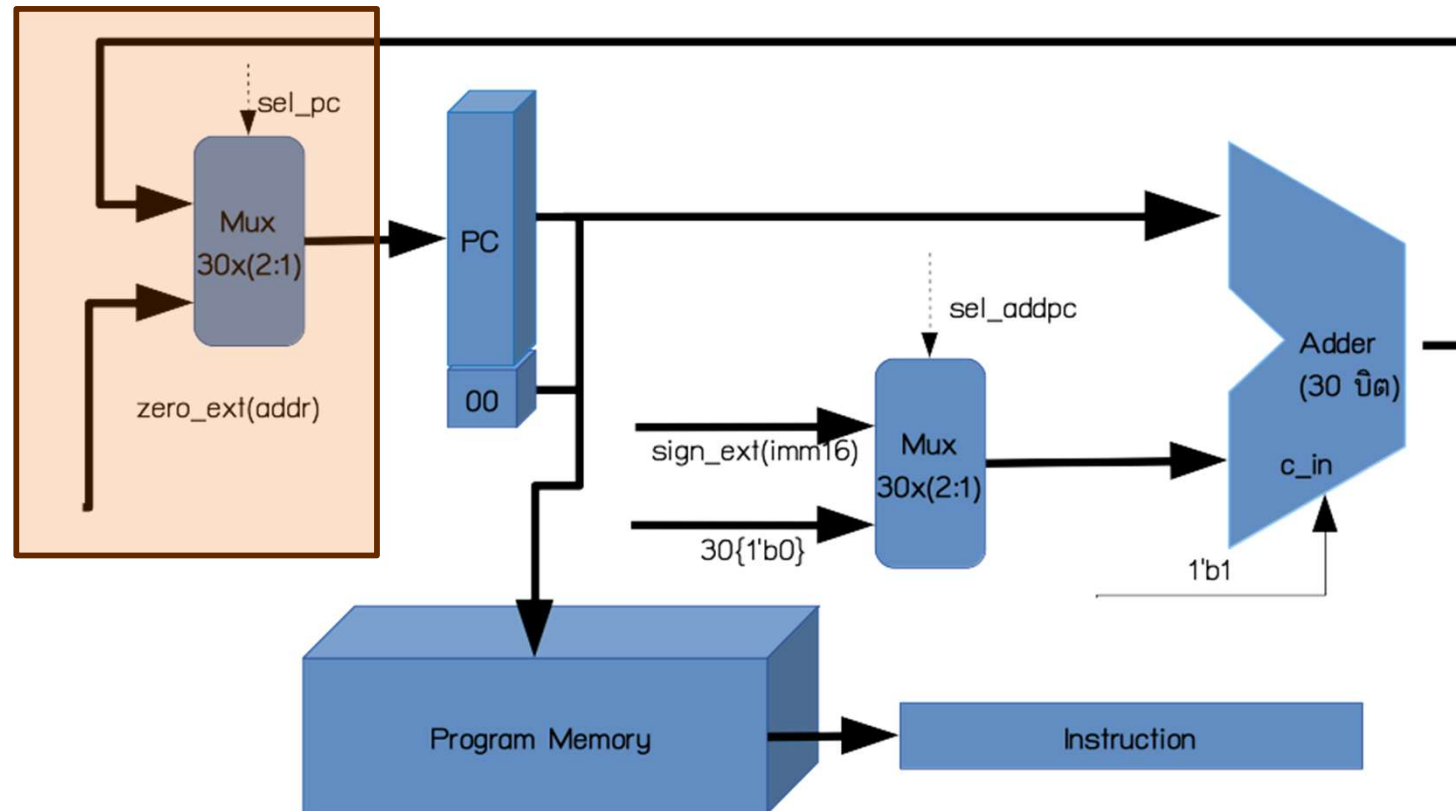
# JMP

★ JMP  $\text{addr} * 4$  ; (J-type)


- $\text{PC} \leftarrow (\text{addr} * 4)$




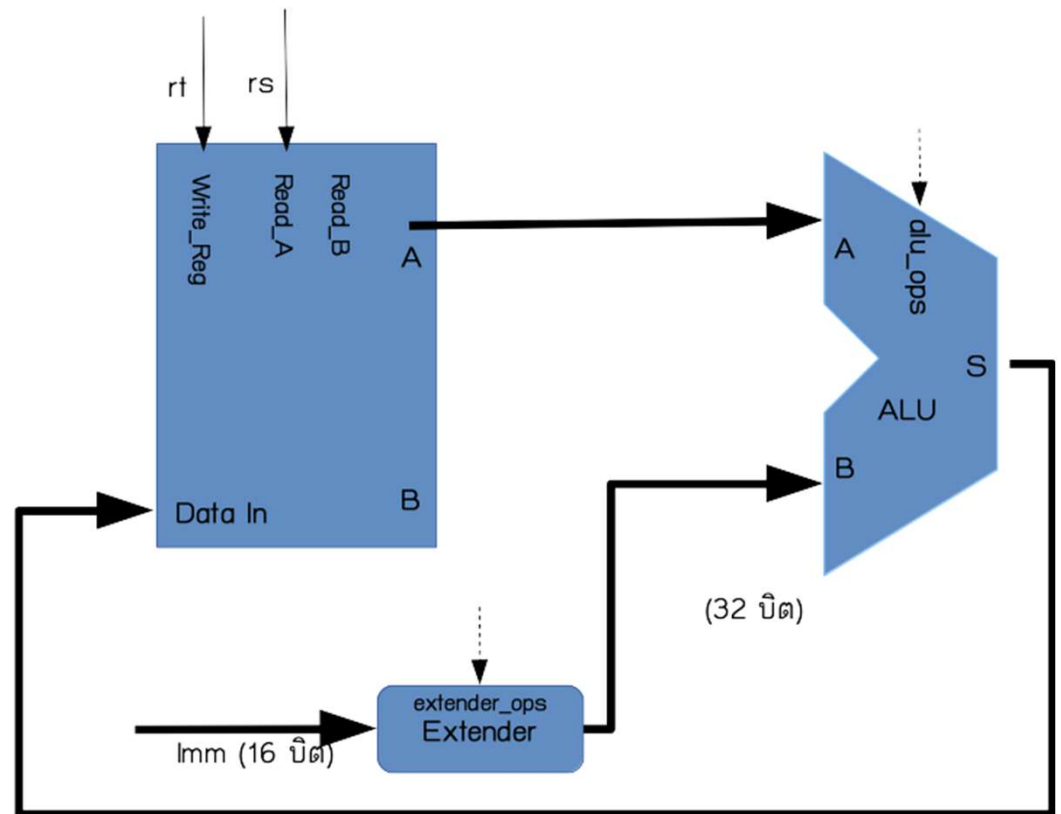
# ORI, ORUI


- ★ ORI  $rt, rs, imm$  ; (I-type)
  - $R[rt] \leftarrow R[rs] \mid \text{zero\_ext}(imm);$   
 $PC \leftarrow PC + 4$
- ★ ORUI  $rt, rs, imm$  ; (I-type)
  - $R[rt] \leftarrow R[rs] \mid \text{zero\_pad}(imm);$   
 $PC \leftarrow PC + 4$
- ★ Same data path, only different extender operation.


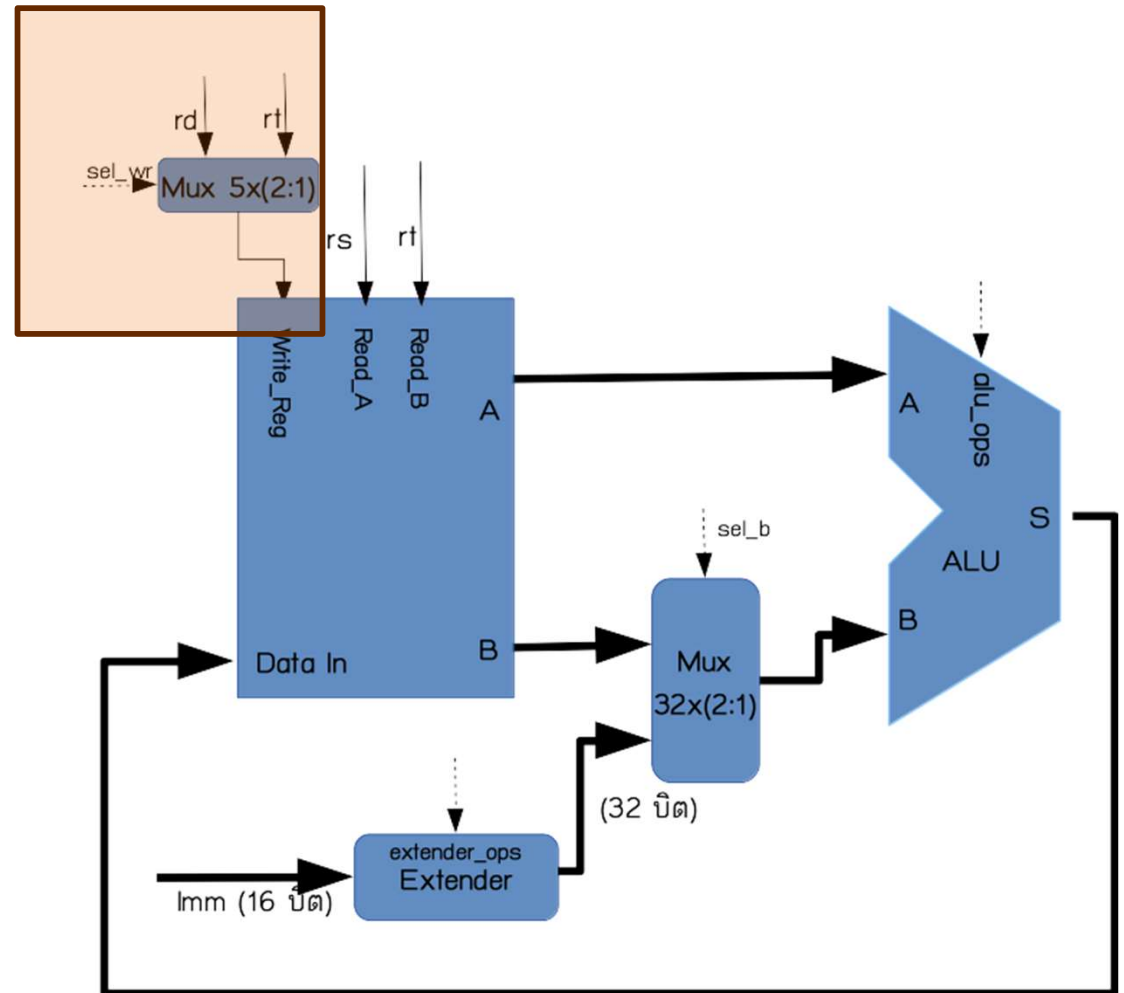
# Add

★ ADD      rd, rs, rt ; (R-type)

- $R[rd] \leftarrow R[rs] + R[rt];$   
 $PC \leftarrow PC + 4$






# LW

★ LW rt, imm(rs)

; (I-type)

- $R[rt] \leftarrow MEM[R[rs] + \text{sign\_ext}(\text{imm})];$


$PC \leftarrow PC + 4$

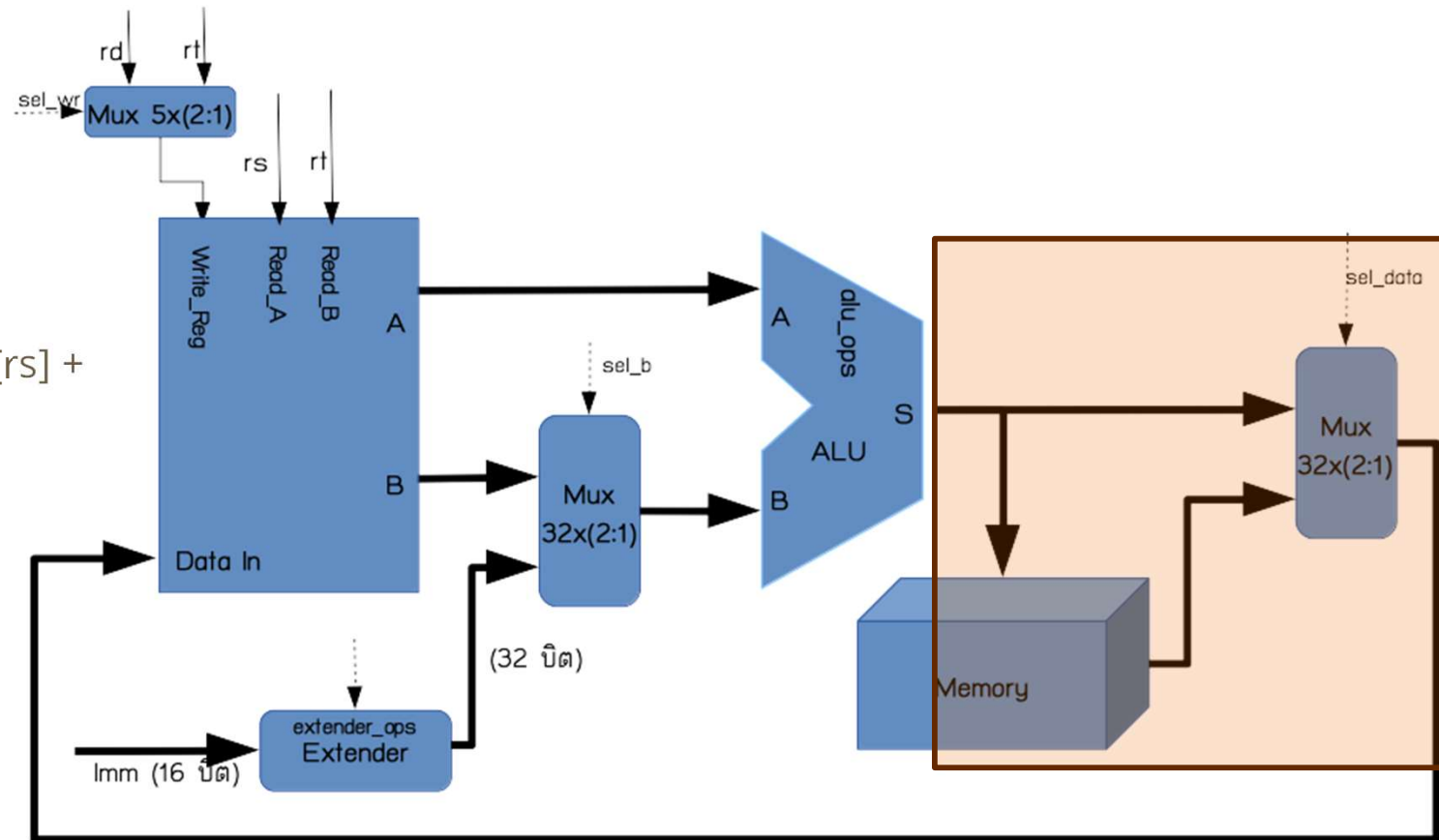


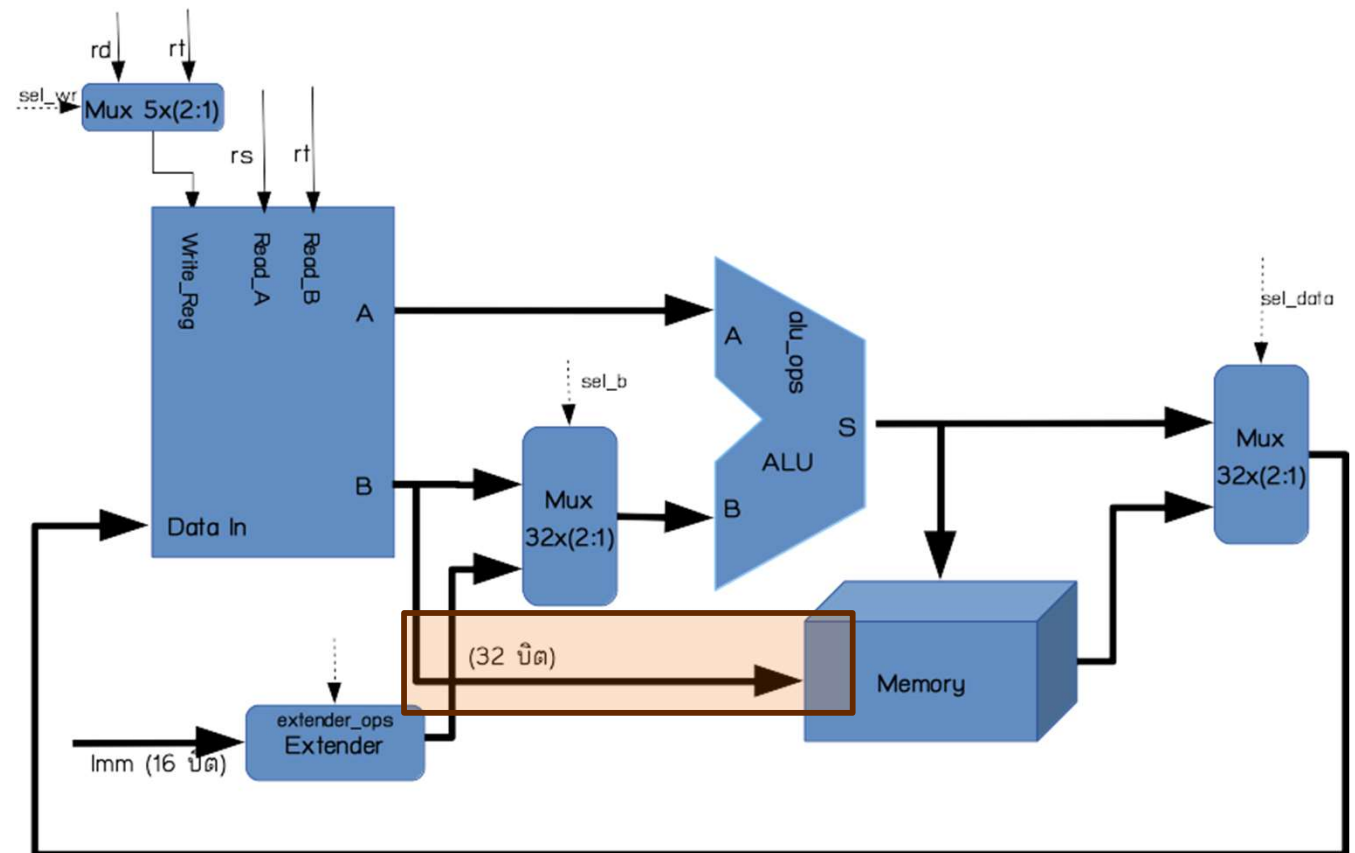
# SW


- ★ SW  $rt, imm(rs)$   
; (l-type)
  - $MEM[R[rs] + sign\_ext(imm)] \leftarrow R[rt];$
  - $PC \leftarrow PC + 4$







# Complete Data Path

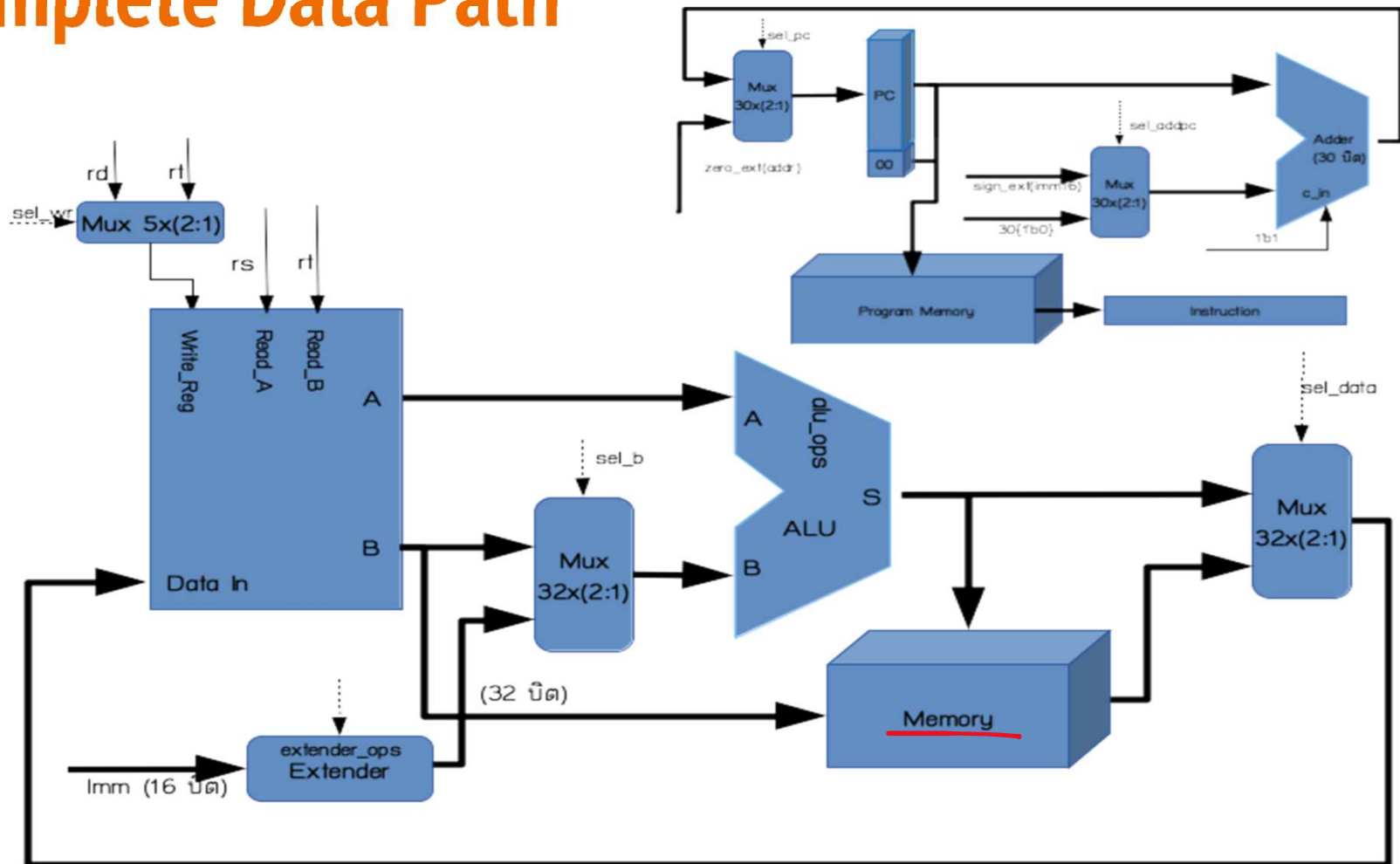



## Step 4: RTL > Control (for the given datapath)

### ★ Control Signals

- sel\_pc
- sel\_addpc
- sel\_wr
- sel\_b
- sel\_data
- reg\_wr
- Mem\_wr
- alu\_ops



# Step 5: Control

Opcode	Zero (ALU)	sel_pc 0 - PC 1 - addr	sel_addpc 0 - 0 1 - addr	sel_wr 0 - rd 1 - rt	sel_b 0 - R[rt] 1 - imm	sel_data 0 - S 1 - M	reg_wr 1 - wr	mem_wr 1 - wr	alu_ops
ORI 010000	x	0	0	1	0	0	0	0	01
ORUI 010001	x	0	0	1	0	0	0	0	01
ADD 000001	x	0	0	0	0	0	0	0	00
LW 011000	x	0	0	1	1	1	0	0	00
SW 01100	x	0	0	x	1	x	0	1	00
BEQ 100100	0 1	0 0	0 1	x	x	x	0	0	10
JMP 110000	x	1	x	x	x	x	0	0	00




# Control Implementation

- ★ Combinational Logic
- ★ ROM
- ★ PLA
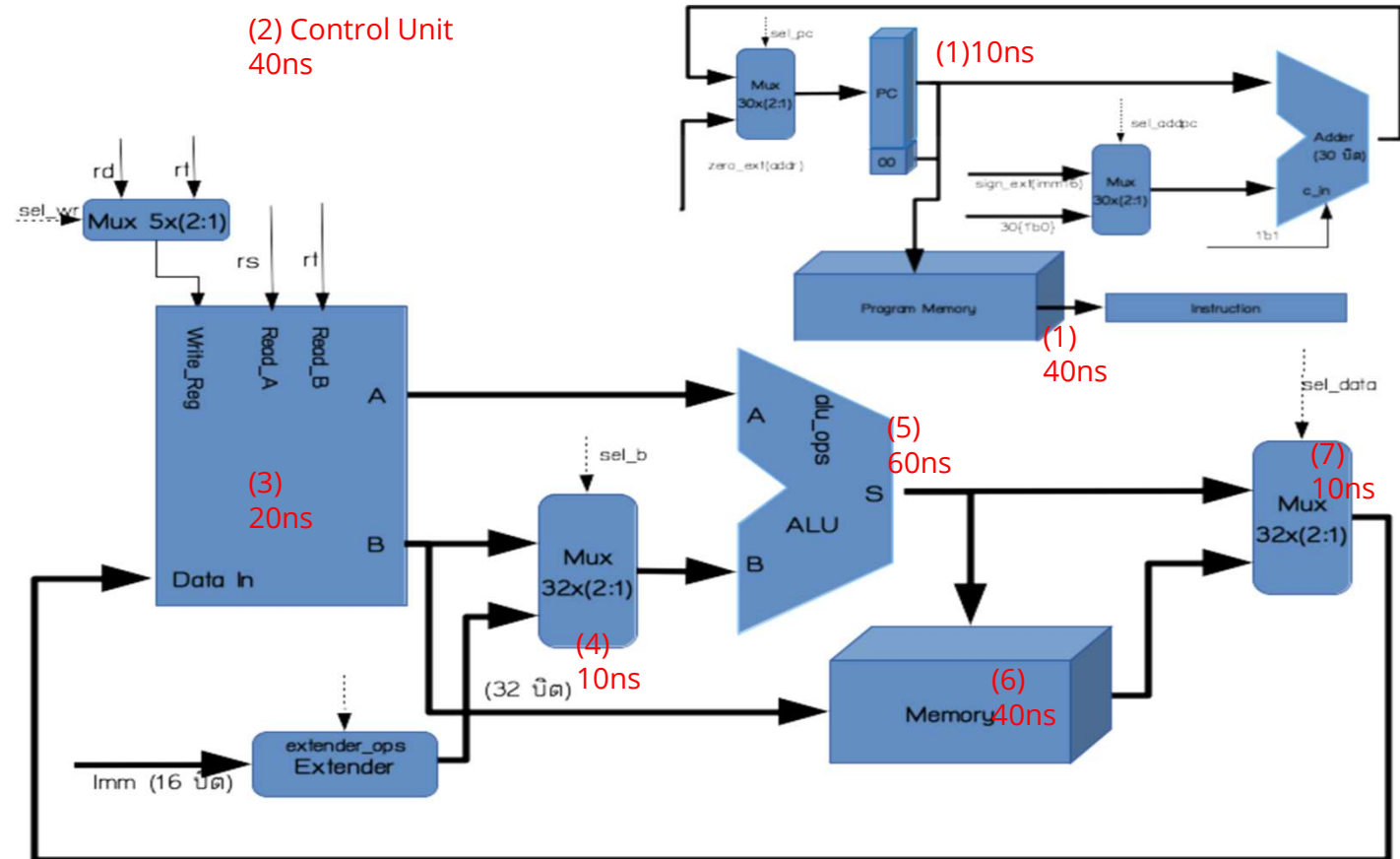
# Critical Path

$$(1) 10 + 40 + (2) 40 + (3) 20 + (4) 10 + (5) 60 + (6) 40 + (7) 10$$

- ★ Longest path?
- ★ Instruction ← MEM[PC]
  - PC 10ns
  - MEM 40ns
- ★ Control/Decode 40ns
- ★ Register 20ns
- ★ Extender 10ns
- ★ MUX 10ns
- ★ ALU 60ns
- ★ MUX 10ns





# Summary

- ★ The simplicity of nanoLADA makes it easy.
  - Few instructions
  - Fixed-Length instruction set
  - Immediate and Location (Displacement) share the same field.
- ★ Single Cycle datapath
  - CPI=1
  - Cycle Time - Long
- ★ How to make it faster?



**Given an ISA, can you design datapath?**





# Exercises







# Performance

- ★ For the given single cycle processor, if a benchmark contains 2 millions instructions, calculate the CPU time.

Assuming that the critical path is 230 ns.



$$\text{clock rate} = \frac{10^9}{230} = 4.35 \times 10^6 \text{ Hz}$$



# ALU

★ Please design an ALU that supports the following operations

alu_ops	Operation
00	$S \leftarrow A + B ; z \leftarrow (S == 0)$
01	$S \leftarrow A   B ; z \leftarrow (S == 0)$
10	$S \leftarrow A - B ; z \leftarrow (S == 0)$

 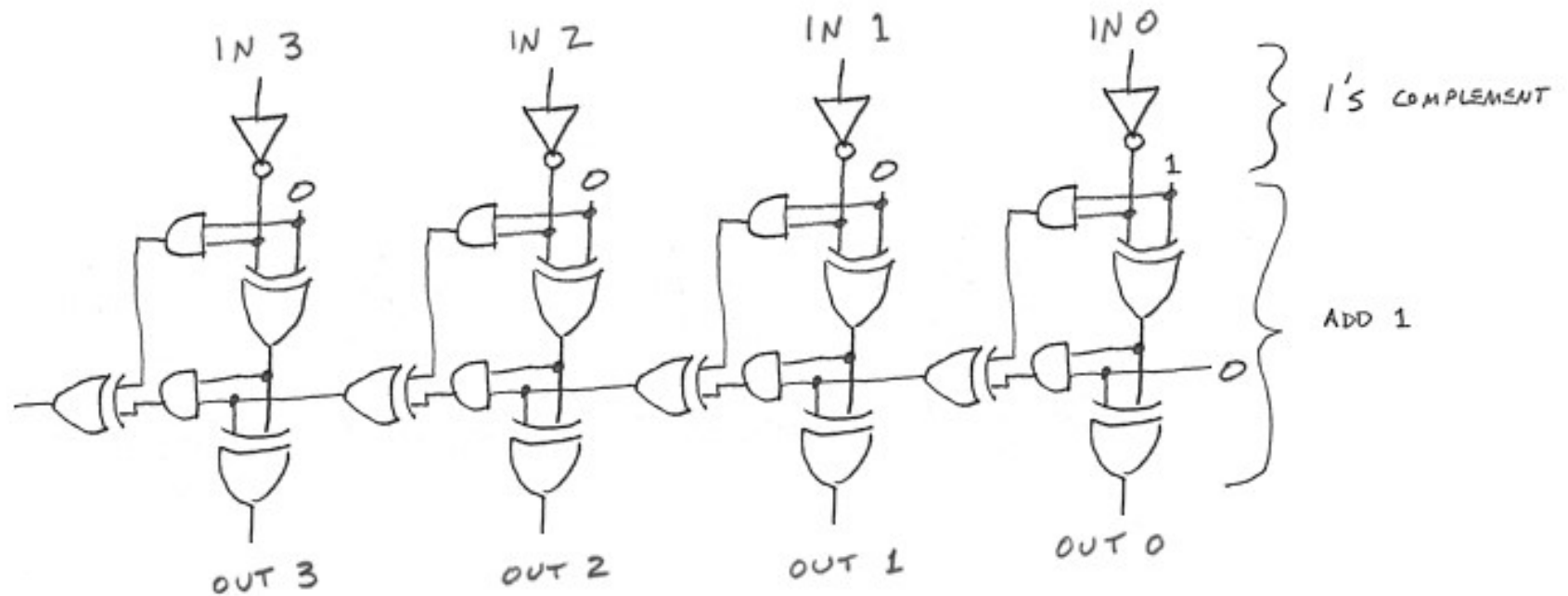

[https://cs.stackexchange.com/questions/51034/twos-complement-using-only-](https://cs.stackexchange.com/questions/51034/twos-complement-using-only-logic-gates)

Computer Architecture: Design and Analysis

logic-gates

Krerk Piromsopa, Ph.D. @ 2016



# PLA Implementation

★ How to implement the control signal (in p.26) with PLA?

G1 represents ORI (010000) -  $G1 = x_5^1 x_4 x_3^1 x_2^1 x_1^1 x_0^1$

G2 represents ORUI (010001) -  $G2 = x_5^1 x_4 x_3^1 x_2^1 x_1^1 x_0^0$

G3 represents ADD (000001) -  $G3 = x_5^1 x_4^1 x_3^1 x_2^1 x_1^1 x_0^0$

G4 represents LW (011000) -  $G4 = x_5^1 x_4 x_3 x_2^1 x_1^1 x_0^1$

G5 represents SW (011100) -  $G5 = x_5^1 x_4 x_3 x_2 x_1^1 x_0^1$

G6 represents BEQ (100100) -  $G6 = x_5 x_4^1 x_3^1 x_2 x_1^1 x_0^1$

G7 represents JMP (110000) -  $G7 = x_5 x_4 x_3^1 x_2^1 x_1^1 x_0^1$

$sel\_pc = G7$

$sel\_addpc = G6 + zero$

$sel\_wr = G1 + G2 + G4$

$sel\_b = G1 + G2 + G4 + G5$

$sel\_data = G4$

$reg\_wr = G1 + G2 + G3 + G4$

$mem\_wr = G5$



# Adding scale operation

- Scale      LD \$r1, (\$r2)[\$r3\*4]



## End of Chapter 4

