

CEDT

2110252 Digital Computer Logic


Chap07 Finite State Machine

Finite State Machines

- Sequential circuits
 - primitive sequential elements
 - combinational logic
- Models for representing sequential circuits
 - finite-state machines (Moore and Mealy)
- Basic sequential circuits revisited
 - shift registers
 - counters
- Design procedure
 - state diagrams
 - state transition table
 - next state functions
- Hardware description languages


Abstraction of state elements

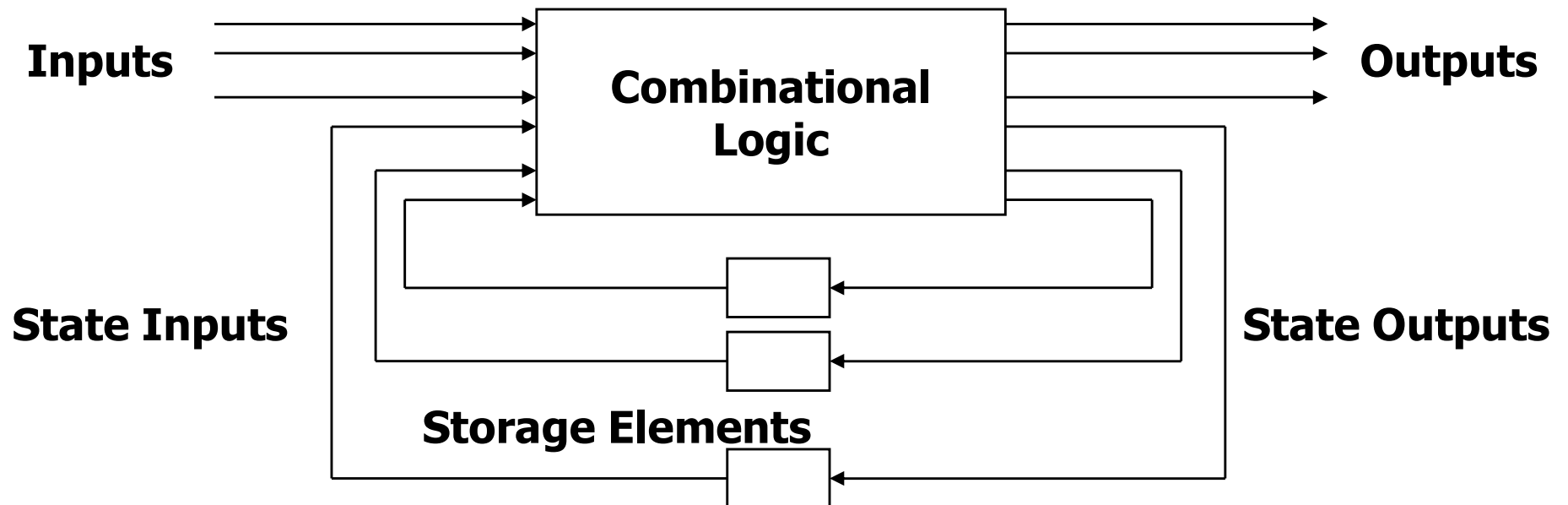- Divide circuit into combinational logic and state
- Localize the feedback loops and make it easy to break cycles
- Implementation of storage elements leads to various forms of sequential logic




Forms of sequential logic

 - Asynchronous sequential logic – state changes occur whenever state inputs change (elements may be simple wires or delay elements)
- Synchronous sequential logic – state changes occur in lock step across all storage elements (using a periodic waveform - the clock)




Finite state machine representations

 - States: determined by possible values in sequential storage elements
- Transitions: change of state
- Clock: controls when state can change by controlling storage elements
- Sequential logic
 - sequences through a series of states
 - based on sequence of values on input signals
 - clock period defines elements of sequence



 Example finite state machine diagram



- Combination lock from introduction to course
 - 5 states
 - 5 self-transitions
 - 6 other transitions between states
 - 1 reset transition (from all states) to state S1



Can any sequential system be represented with a state diagram?

■ Shift register

  - input value shown on transition arcs
- output values shown within state node




Counters are simple finite state machines

■ Counters

- proceed through well-defined sequence of states in response to enable


■ Many types of counters: binary, BCD, Gray-code

 - 3-bit up-counter: 000, 001, 010, 011, 100, 101, 110, 111, 000, ...
- 3-bit down-counter: 111, 110, 101, 100, 011, 010, 001, 000, 111, ...



How do we turn a state diagram into logic?

 - Counter
 - 3 flip-flops to hold state
 - logic to compute next state
 - clock signal controls when flip-flop memory can change
 - wait long enough for combinational logic to compute new value
 - don't wait too long as that is low performance




FSM design procedure

- Start with counters
 - simple because output is just state
 - simple because no choice of next state based on input

- State diagram to state transition table
 - tabular form of state diagram
 - like a truth-table
- State encoding
 - decide on representation of states
 - for counters it is simple: just its value
- Implementation
 - flip-flop for each state bit
 - combinational logic based on encoding

FSM design procedure: state diagram to encoded state transition table

 - Tabular form of state diagram
- Like a truth-table (specify output for all input combinations)
- Encoding of states: easy for counters – just use value



present state		next state	
0	000	001	1
1	001	010	2
2	010	011	3
3	011	100	4
4	100	101	5
5	101	110	6
6	110	111	7
7	111	000	0

Implementation

present state		next state	
0	000	001	1
1	001	010	2
2	010	011	3
3	011	100	4
4	100	101	5
5	101	110	6
6	110	111	7
7	111	000	0

- D flip-flop for each state bit
- Combinational logic based on encoding

C3	C2	C1	N3	N2	N1
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

Verilog notation to show function represents an input to D-FF

$N1 \leq C1'$
 $N2 \leq C1C2' + C1'C2$
 $\leq C1 \text{ xor } C2$
 $N3 \leq C1C2C3' + C1'C3 + C2'C3$
 $\leq (C1C2)C3' + (C1' + C2')C3$
 $\leq (C1C2)C3' + (C1C2)'C3$
 $\leq (C1C2) \text{ xor } C3$

N3

	C3			
	0	0	1	1
C1	0	1	0	1
	C2			

N2

	C3			
	0	1	1	0
C1	1	0	0	1
	C2			


N1

	C3			
	1	1	1	1
C1	0	0	0	0
	C2			

Implementation

C3	C2	C1	N3	N2	N1
0	0	0	0	0	1
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	1
1	0	1	1	1	0
1	1	0	1	1	1
1	1	1	0	0	0

 
$N1 \leq C1'$
 $\leq 1 \text{ xor } C1$
 $N2 \leq C1C2' + C1'C2$
 $\leq C1 \text{ xor } C2$
 $N3 \leq C1C2C3' + C1'C3 + C2'C3$
 $\leq (C1C2)C3' + (C1' + C2')C3$
 $\leq (C1C2)C3' + (C1C2)'C3$
 $\leq (C1C2) \text{ xor } C3$




Back to the shift register

- Input determines next state

In	C1	C2	C3	N1	N2	N3
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	0	1	0
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	0	1	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	1	0	1
1	0	1	1	1	0	1
1	1	0	0	1	1	0
1	1	0	1	1	1	0
1	1	1	0	1	1	1
1	1	1	1	1	1	1

 


$N1 \leq In$
 $N2 \leq C1$
 $N3 \leq C2$

 

More complex counter example

 - Complex counter
 - repeats 5 states in sequence
 - not a binary number representation
- Step 1: derive the state transition diagram
 - count sequence: 000, 010, 011, 101, 110
- Step 2: derive the state transition table from the state transition diagram



Present State			Next State		
C	B	A	C+	B+	A+
0	0	0	0	1	0
0	0	1	—	—	—
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	—	—	—
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	—	—	—

note the don't care conditions that arise from the unused state codes

More complex counter example (cont'd)

- Step 3: K-maps for next state functions

Present State			Next State		
C	B	A	C+	B+	A+
0	0	0	0	1	0
0	0	1	—	—	—
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	—	—	—
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	—	—	—

C+		C			
		0	0	0	X
A		X	1	X	1
		B			

B+		C		
	1	1	0	X
A	X	0	X	1
	B			

A+		C		
	0	1	0	X
A	X	1	X	0
	B			

$$C+ \leq A$$

$$B+ \leq B' + A'C'$$

$$A+ \leq BC'$$

Self-starting counters (cont'd)


- Re-deriving state transition table from don't care assignment

C+		C	
	0	0	0
	0	0	0
A	1	1	1
	B		

B+		C	
	1	1	0
	1	0	1
A	1	0	0
	B		

A+		C	
	0	1	0
	0	1	0
A	0	1	0
	B		

Present State			Next State		
C	B	A	C+	B+	A+
0	0	0	0	1	0
0	0	1	1	1	0
0	1	0	0	1	1
0	1	1	1	0	1
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	0	0	0
1	1	1	1	0	0

 



Self-starting counters

■ Start-up states

- ❑ at power-up, counter may be in an unused or invalid state
- ❑ designer must guarantee that it (eventually) enters a valid state

■ Self-starting solution

  - ❑ design counter so that invalid states eventually transition to a valid state
- ❑ may limit exploitation of don't cares




Activity

- 2-bit up-down counter (2 inputs)
 - direction: $D = 0$ for up, $D = 1$ for down
 - count: $C = 0$ for hold, $C = 1$ for count

Activity (cont'd)


Counter/shift-register model

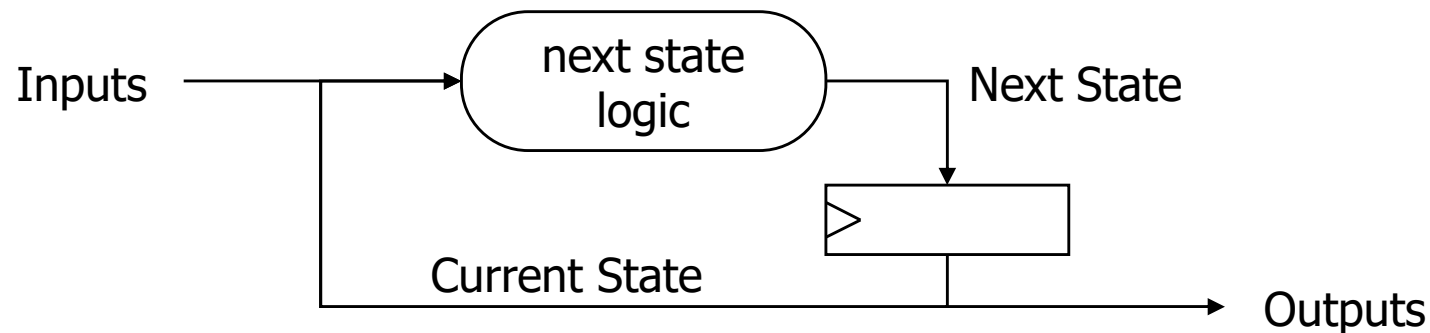- Values stored in registers represent the state of the circuit
- Combinational logic computes:
 - next state
 - function of current state and inputs
 - outputs
 - values of flip-flops





General state machine model

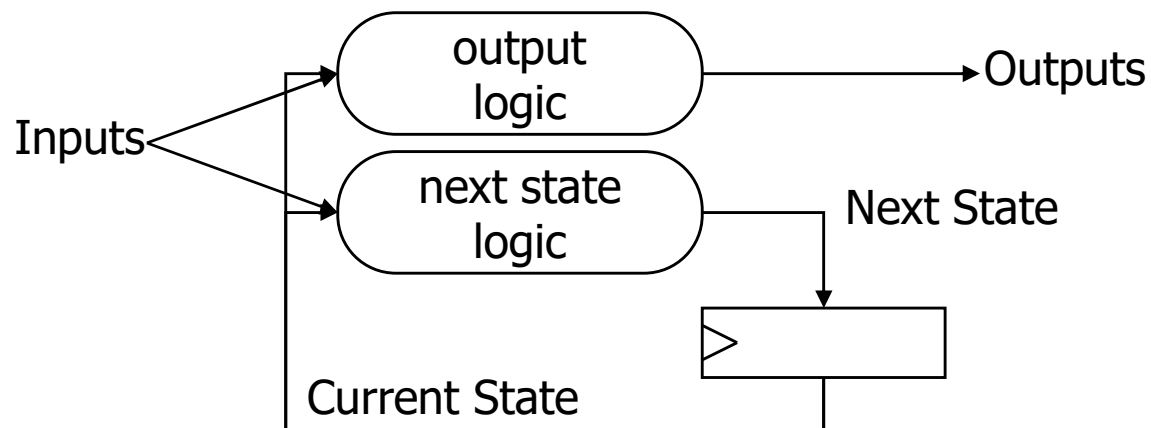- Values stored in registers represent the state of the circuit
- Combinational logic computes:
 - next state
 - function of current state and inputs
 - outputs
 - function of current state and inputs (Mealy machine)
 - function of current state only (Moore machine)



State machine model (cont'd)

 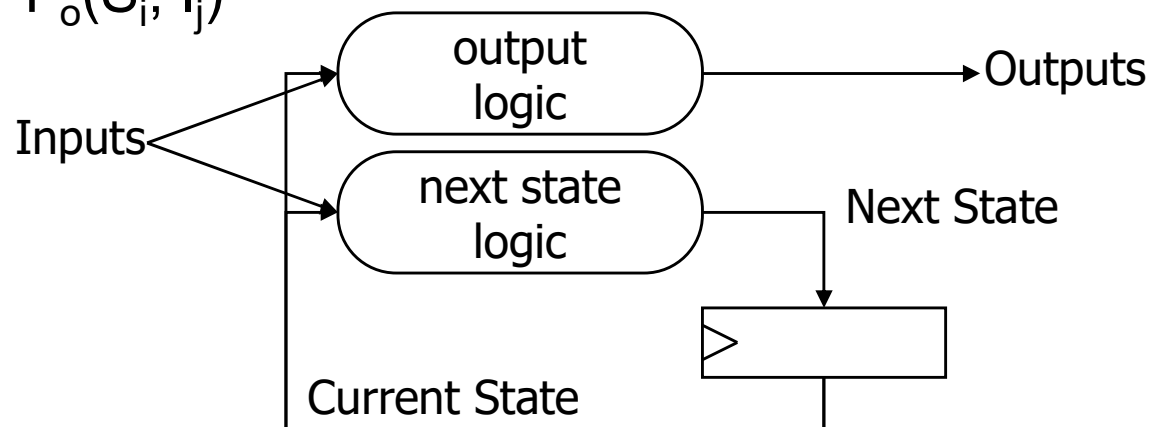- States: S_1, S_2, \dots, S_k
- Inputs: I_1, I_2, \dots, I_m
- Outputs: O_1, O_2, \dots, O_n
- Transition function: $F_s(S_i, I_j)$
- Output function: $F_o(S_i)$ or $F_o(S_i, I_j)$




Comparison of Mealy and Moore machines


- Mealy machines tend to have less states
 - different outputs on arcs (n^2) rather than states (n)
- Moore machines are safer to use
 - outputs change at clock edge (always one cycle later)
 - in Mealy machines, input change can cause output change as soon as logic is done – a big problem when two machines are interconnected – asynchronous feedback may occur if one isn't careful
- Mealy machines react faster to inputs
 - react in same cycle – don't need to wait for clock
 - in Moore machines, more logic may be necessary to decode state into outputs – more gate delays after clock edge

Comparison of Mealy and Moore machines (cont'd)


■ Moore

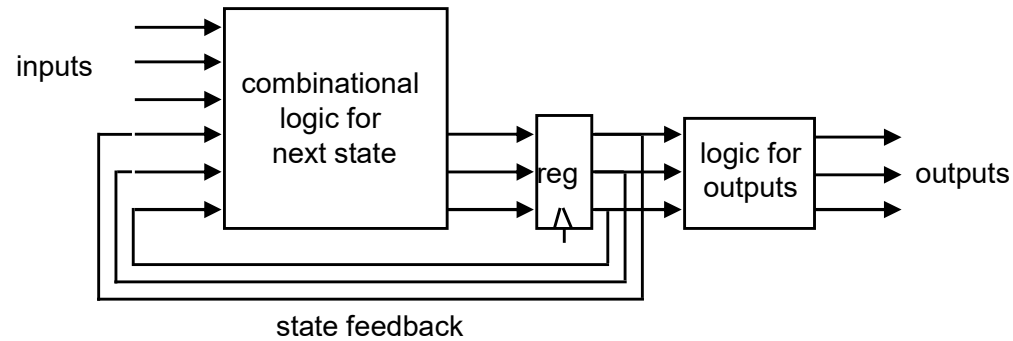

■ Mealy

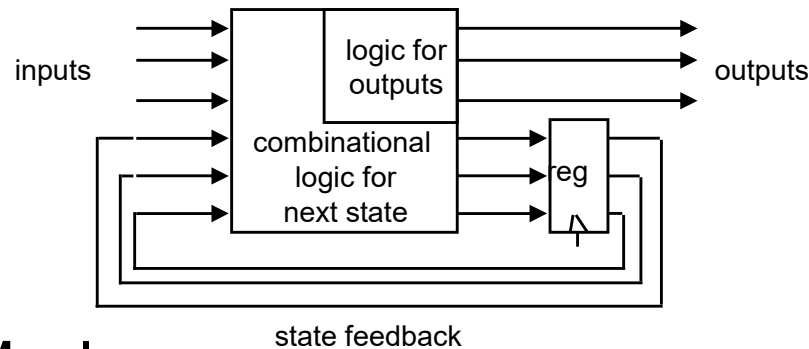


■ Synchronous Mealy

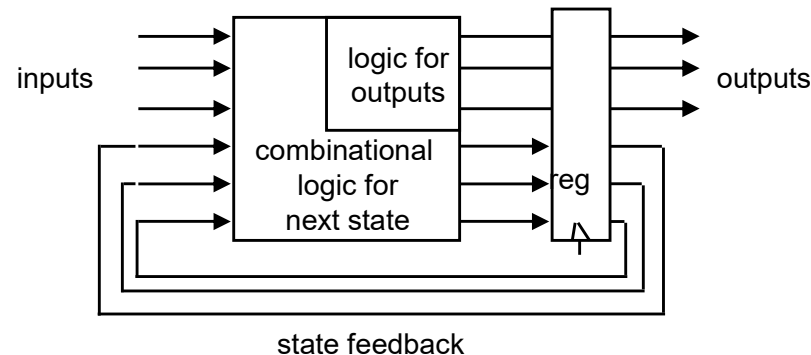

Specifying outputs for a Moore machine

 
- Output is only function of state
 - specify in state bubble in state diagram
 - example: sequence detector for 01 or 10



reset	input	current state	next state	output
1	—	—	A	
0	0	A	B	0
0	1	A	C	0
0	0	B	B	0
0	1	B	D	0
0	0	C	E	0
0	1	C	C	0
0	0	D	E	1
0	1	D	C	1
0	0	E	B	1
0	1	E	D	1

Specifying outputs for a Mealy machine

 
- Output is function of state and inputs
 - specify output on transition arc between states
 - example: sequence detector for 01 or 10



reset	input	current state	next state	output
1	—	—	A	0
0	0	A	B	0
0	1	A	C	0
0	0	B	B	0
0	1	B	C	1
0	0	C	B	1
0	1	C	C	0


Registered Mealy machine (really Moore)

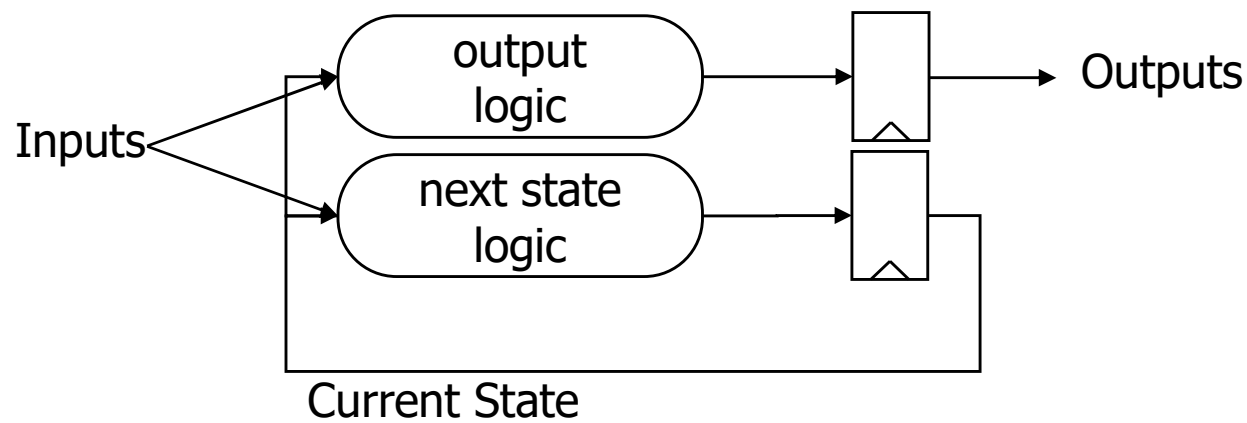- Synchronous (or registered) Mealy machine
 - registered state AND outputs
 - avoids 'glitchy' outputs
 - easy to implement in PLDs (Programmable logic devices)
- Moore machine with no output decoding
 - outputs computed on transition to next state rather than after entering
 - view outputs as expanded state vector



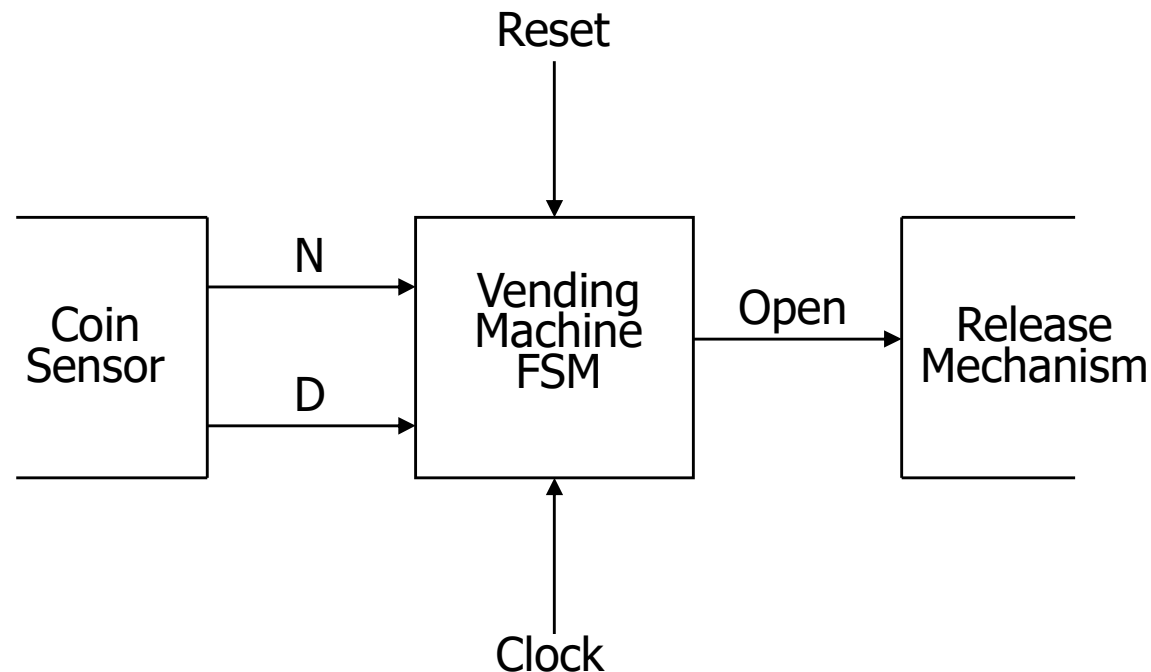Example: vending machine

- Release item after 15 cents are deposited
- Single coin slot for dimes (10 cents), nickels (5 cents)
- No change



Example: vending machine (cont'd)

■ Suitable abstract representation

□ tabulate typical input sequences:


- 3 nickels
- nickel, dime
- dime, nickel
- two dimes

□ draw state diagram:

- inputs: N, D, reset
- output: open chute


□ assumptions:

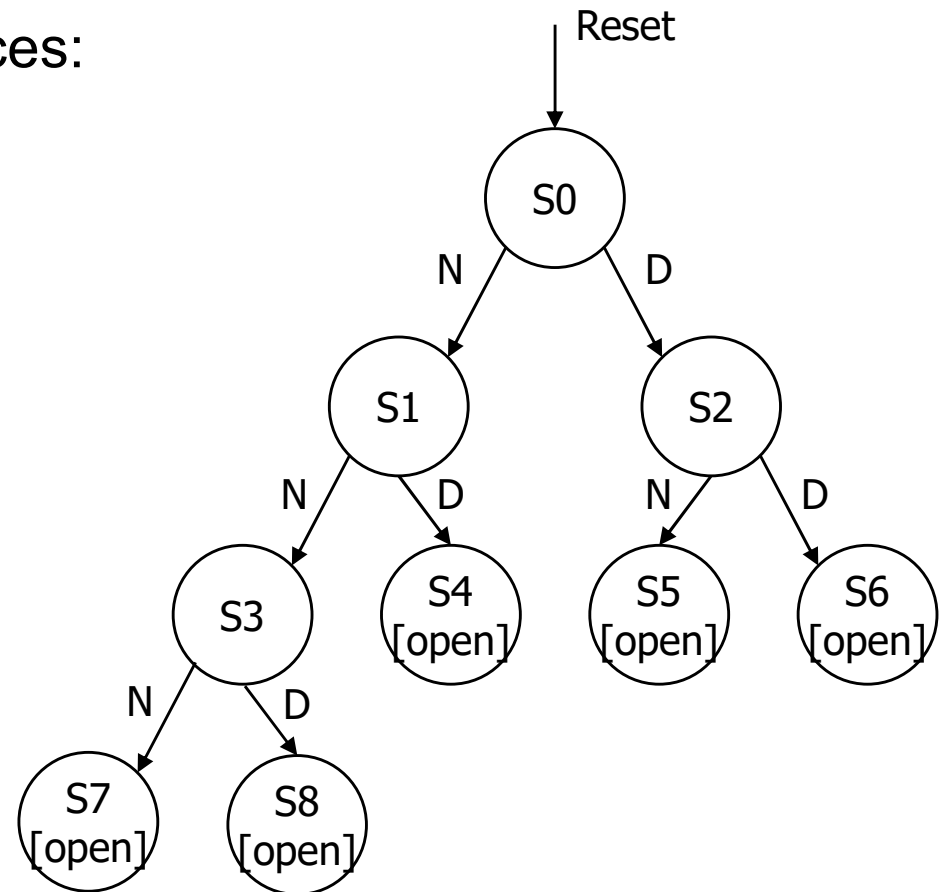- assume N and D asserted for one cycle
- each state has a self loop for $N = D = 0$ (no coin)



 Example: vending machine (cont'd)

- Minimize number of states - reuse states whenever possible



present state	inputs		next state	output open
	D	N		
0¢	0	0	0¢	0
	0	1	5¢	0
	1	0	10¢	0
	1	1	—	—
5¢	0	0	5¢	0
	0	1	10¢	0
	1	0	15¢	0
	1	1	—	—
10¢	0	0	10¢	0
	0	1	15¢	0
	1	0	15¢	0
	1	1	—	—
15¢	—	—	15¢	1

symbolic state table

Example: vending machine (cont'd)


- Uniquely encode states

present state		inputs		next state		output
Q1	Q0	D	N	D1	D0	open
0	0	0	0	0	0	0
		0	1	0	1	0
		1	0	1	0	0
		1	1	—	—	—
0	1	0	0	0	1	0
		0	1	1	0	0
		1	0	1	1	0
		1	1	—	—	—
1	0	0	0	1	0	0
		0	1	1	1	0
		1	0	1	1	0
		1	1	—	—	—
1	1	—	—	1	1	1


present state	inputs		next state	output
	D	N		open
0¢	0	0	0¢	0
	0	1	5¢	0
	1	0	10¢	0
	1	1	—	—
5¢	0	0	5¢	0
	0	1	10¢	0
	1	0	15¢	0
	1	1	—	—
10¢	0	0	10¢	0
	0	1	15¢	0
	1	0	15¢	0
	1	1	—	—
15¢	—	—	15¢	1

Example: Moore implementation

■ Mapping to logic

 

present state		inputs		next state		output
Q1	Q0	D	N	D1	D0	open
0	0	0	0	0	0	0
		0	1	0	1	0
		1	0	1	0	0
		1	1	—	—	—
0	1	0	0	0	1	0
		0	1	1	0	0
		1	0	1	1	0
		1	1	—	—	—
1	0	0	0	1	0	0
		0	1	1	1	0
		1	0	1	1	0
		1	1	—	—	—
1	1	—	—	1	1	1

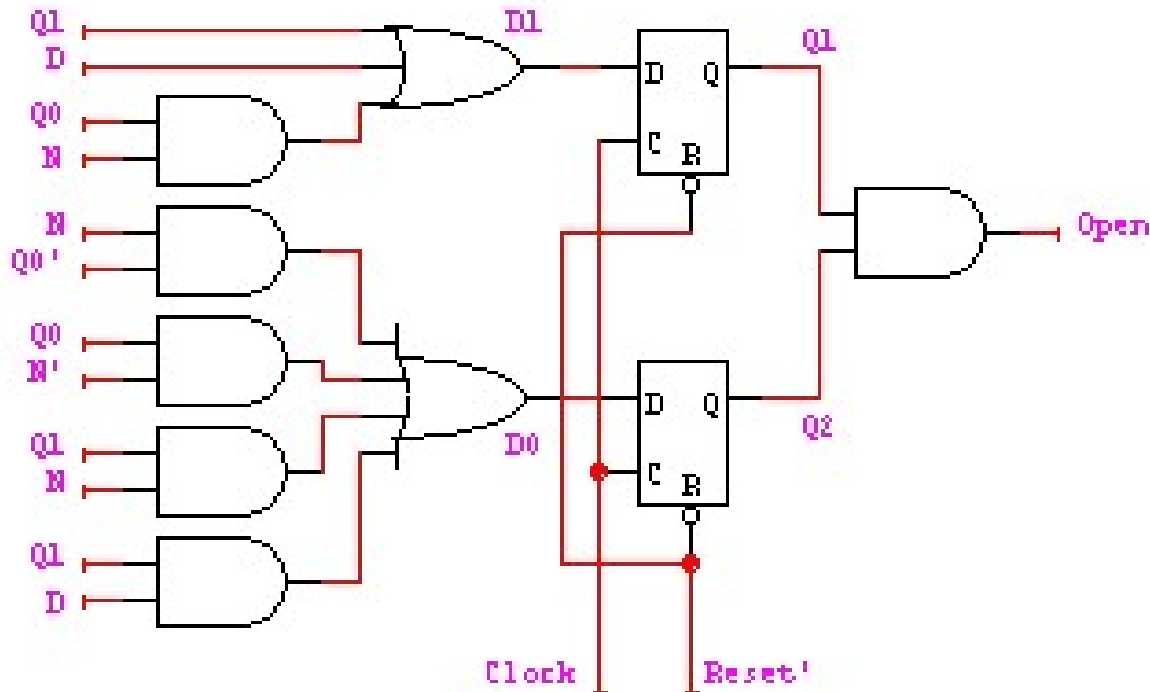

$$D1 = Q1 + D + Q0 N$$

$$D0 = Q0' N + Q0 N' + Q1 N + Q1 D$$

$$OPEN = Q1 Q0$$

Example: vending machine (cont'd)

■ One-hot encoding

present state				inputs		next state				output
Q3	Q2	Q1	Q0	D	N	D3	D2	D1	D0	open
0	0	0	1	0	0	0	0	0	1	0
				0	1	0	0	1	0	0
				1	0	0	1	0	0	0
				1	1	-	-	-	-	-
0	0	1	0	0	0	0	0	1	0	0
				0	1	0	1	0	0	0
				1	0	1	0	0	0	0
				1	1	-	-	-	-	-
0	1	0	0	0	0	0	1	0	0	0
				0	1	1	0	0	0	0
				1	0	1	0	0	0	0
				1	1	-	-	-	-	-
1	0	0	0	-	-	1	0	0	0	1

$$D0 = Q0 D' N'$$

$$D1 = Q0 N + Q1 D' N'$$

$$D2 = Q0 D + Q1 N + Q2 D' N'$$


$$D3 = Q1 D + Q2 D + Q2 N + Q3$$

$$OPEN = Q3$$

Equivalent Mealy and Moore state diagrams


■ Moore machine

- outputs associated with state

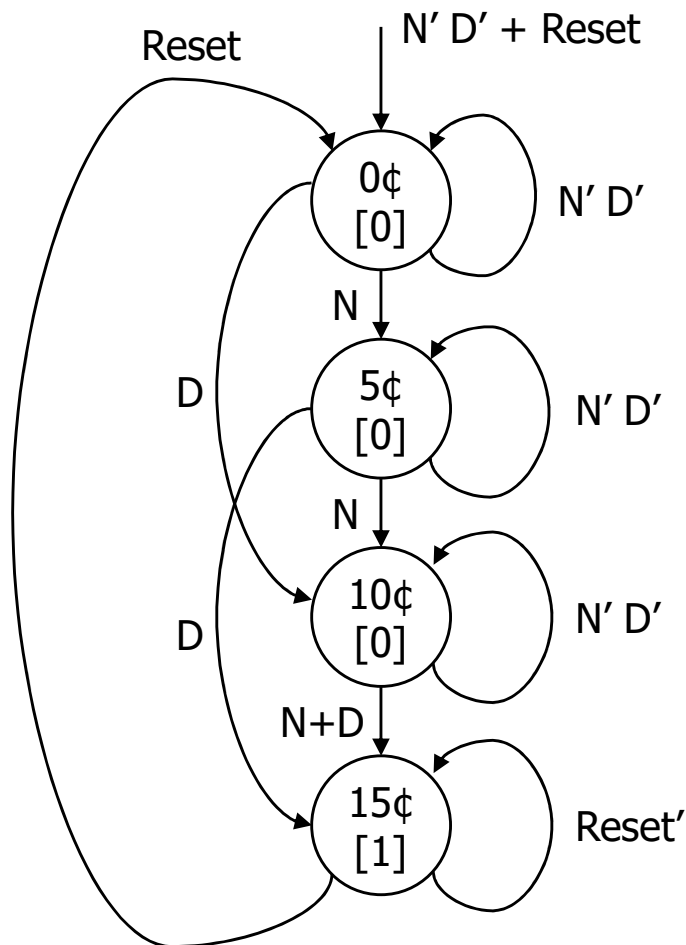


■ Mealy machine

- outputs associated with transitions

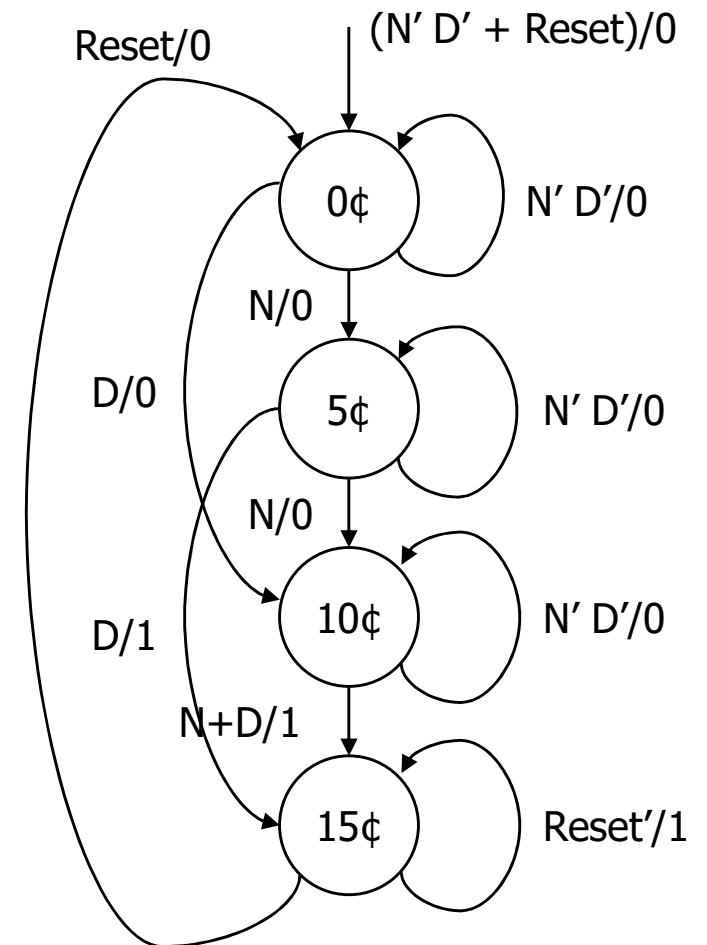

Example: Mealy implementation

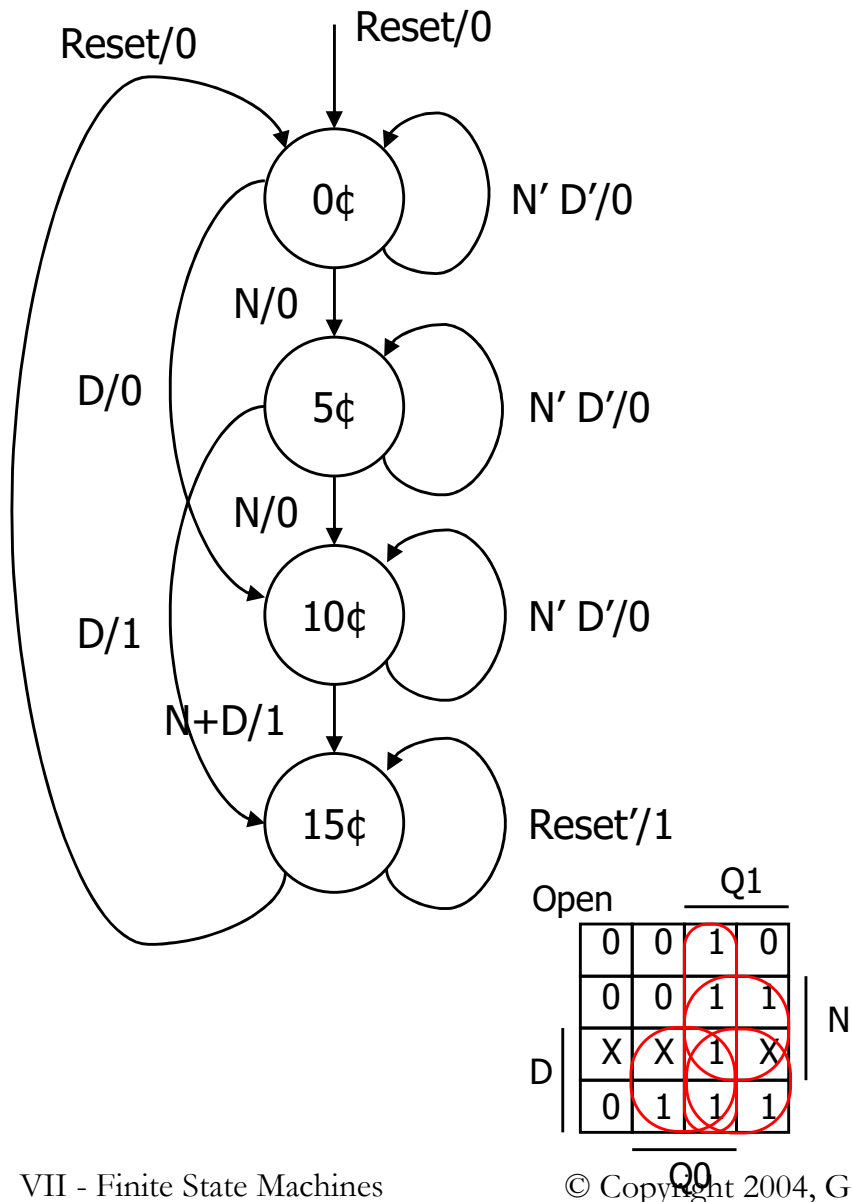

present state		inputs		next state		output
Q1	Q0	D	N	D1	D0	open
0	0	0	0	0	0	0
		0	1	0	1	0
		1	0	1	0	0
		1	1	—	—	—
0	1	0	0	0	1	0
		0	1	1	0	0
		1	0	1	1	1
		1	1	—	—	—
1	0	0	0	1	0	0
		0	1	1	1	1
		1	0	1	1	1
		1	1	—	—	—
1	1	—	—	1	1	1

$$D0 = Q0'N + Q0N' + Q1N + Q1D$$

$$D1 = Q1 + D + Q0N$$

$$OPEN = Q1Q0 + Q1N + Q1D + Q0D$$


Example: Mealy implementation

$$D0 = Q0'N + Q0N' + Q1N + Q1D$$

$$D1 = Q1 + D + Q0N$$



$$\text{OPEN} = Q1Q0 + Q1N + Q1D + Q0D$$

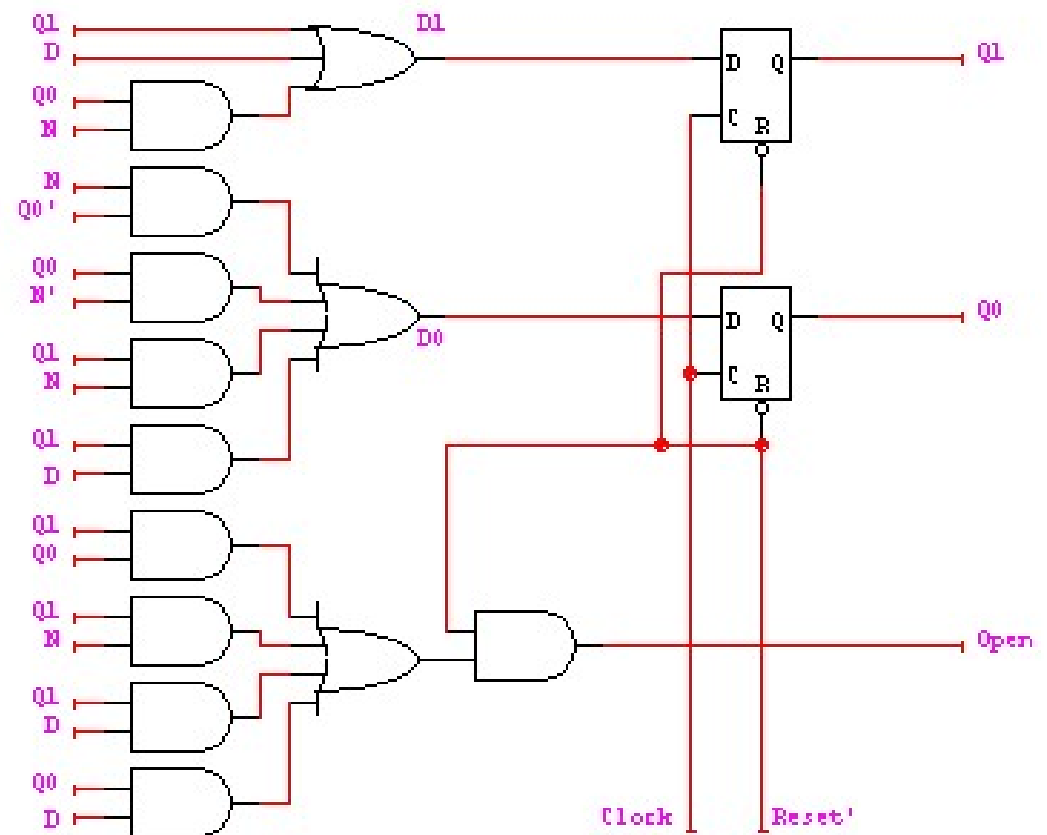make sure OPEN is 0 when reset
– by adding AND gate



Vending machine: Moore to synch. Mealy

- OPEN = Q1Q0 creates a combinational delay after Q1 and Q0 change in Moore implementation
- This can be corrected by retiming, i.e., move flip-flops and logic through each other to improve delay
- $OPEN.d = (Q1 + D + Q0N)(Q0'N + Q0N' + Q1N + Q1D)$
 $= Q1Q0N' + Q1N + Q1D + Q0'ND + Q0N'D$
- Implementation now looks like a synchronous Mealy machine
 - it is common for programmable devices to have FF at end of logic

  


Vending machine: Mealy to synch. Mealy

Mealy ■ OPEN.d = $Q1Q0 + Q1N + Q1D + Q0D$

Synch. ■ OPEN.d = $(Q1 + D + Q0N)(Q0'N + Q0N' + Q1N + Q1D)$

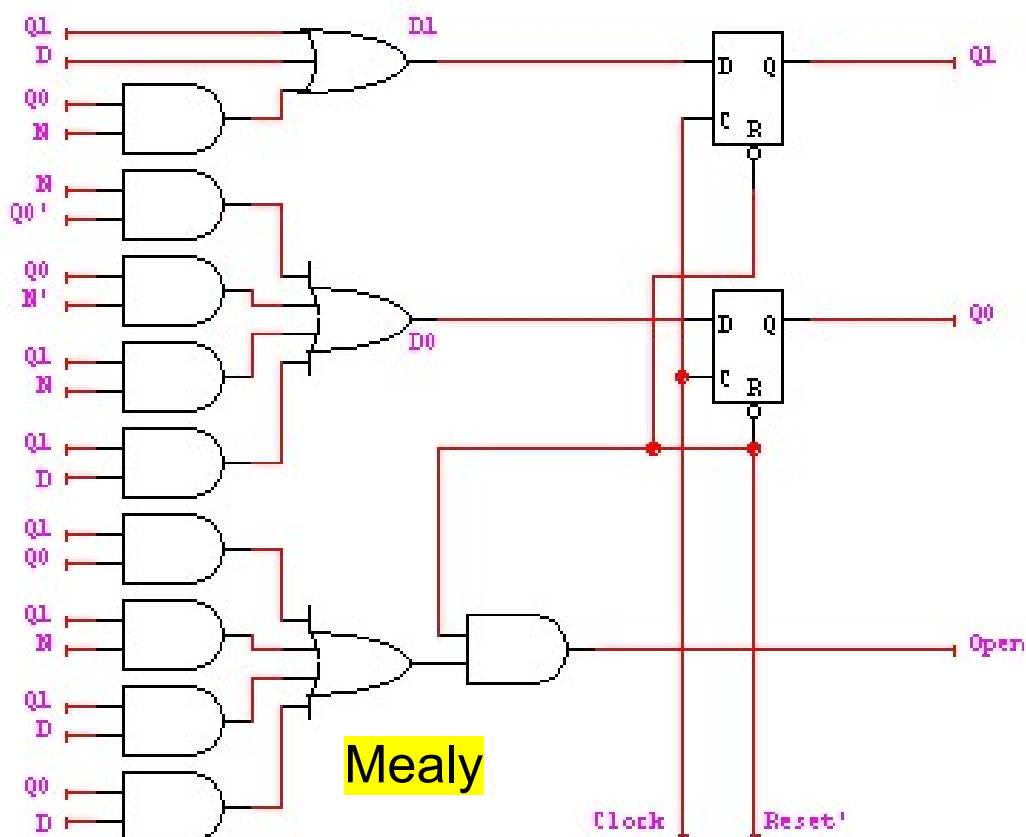Mealy = $Q1Q0N' + Q1N + Q1D + Q0'ND + Q0N'D$



Open.d


	Q1			
	0	0	1	0
D	0	0	1	1
	1	0	1	1
	0	1	1	1
	0	1	1	1

Q0

Open.d




	Q1			
	0	0	1	0
D	0	0	1	1
	X	X	1	X
	0	1	1	1
	0	1	1	1

Q0

 



Mealy and Moore examples

   - Recognize $A, B = 0, 1$
 - Mealy or Moore?



Mealy and Moore examples (cont'd)

  - Recognize A,B = 1,0 then 0,1
 - Mealy or Moore?





Hardware Description Languages and Sequential Logic

- Flip-flops
 - representation of clocks - timing of state changes
 - asynchronous vs. synchronous
- FSMs
 - structural view (FFs separate from combinational logic)
 - behavioral view (synthesis of sequencers – not in this course)
- Data-paths = data computation (e.g., ALUs, comparators) + registers
 - use of arithmetic/logical operators
 - control of storage elements

  Example: reduce-1-string-by-1

- Remove one 1 from every string of 1s on the input




Verilog FSM - Reduce 1s example

■ Moore machine

```
module reduce (clk, reset, in, out);  
  input clk, reset, in;  
  output out;  
  
  parameter zero    = 2'b00;  
  parameter one1    = 2'b01;  
  parameter two1s   = 2'b10;  
  
  reg out;  
  reg [2:1] state;      // state variables  
  reg [2:1] next_state;  
  
  always @(posedge clk)  
    if (reset) state = zero;  
    else      state = next_state;
```

 state assignment
(easy to change,
if in one place)




Moore Verilog FSM (cont'd)


```
always @(in or state)
```

```
    case (state)
        zero:
            // last input was a zero
            begin
                if (in) next_state = one1;
                else    next_state = zero;
            end
        one1:
            // we've seen one 1
            begin
                if (in) next_state = twos;
                else    next_state = zero;
            end
        twos:
            // we've seen at least 2 ones
            begin
                if (in) next_state = twos;
                else    next_state = zero;
            end
    endcase
```

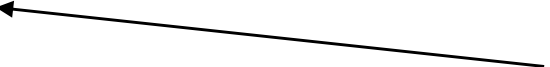crucial to include
all signals that are
input to state determination



note that output
depends only on state



```
always @(state)
    case (state)
        zero: out = 0;
        one1: out = 0;
        twos: out = 1;
    endcase
```


```
endmodule
```

Mealy Verilog FSM

```
module reduce (clk, reset, in, out);
  input clk, reset, in;
  output out;
  reg out;
  reg state; // state variables
  reg next_state;

  always @(posedge clk)
    if (reset) state = zero;
    else      state = next_state;

   always @(in or state)
    case (state)
      zero:           // last input was a zero
      begin
        out = 0;
        if (in) next_state = one;
        else   next_state = zero;
      end
      one:           // we've seen one 1
      if (in) begin
        next_state = one; out = 1;
      end else begin
        next_state = zero; out = 0;
      end
    endcase
endmodule
```



Synchronous Mealy Machine

```
module reduce (clk, reset, in, out);
    input clk, reset, in;
    output out;
    reg out;
    reg state; // state variables

    always @(posedge clk)
        if (reset) state = zero;
        else
            case (state)
                zero: // last input was a zero
                    begin
                        out = 0;
                        if (in) state = one;
                        else state = zero;
                    end
                one: // we've seen one 1
                    if (in) begin
                        state = one; out = 1;
                    end else begin
                        state = zero; out = 0;
                    end
            endcase
    endmodule
```

Finite state machines summary

- Models for representing sequential circuits
 - abstraction of sequential elements
 - finite state machines and their state diagrams
 - inputs/outputs
 - Mealy, Moore, and synchronous Mealy machines
- Finite state machine design procedure
 - deriving state diagram
 - deriving state transition table
 - determining next state and output functions
 - implementing combinational logic